

P2.02

$$i = \frac{5}{100 + 50 \parallel 150} \times \frac{\frac{1}{50}}{\frac{1}{50} + \frac{1}{150}} + 0.1 \times \frac{\frac{1}{50}}{\frac{1}{50} + \frac{1}{100} + \frac{1}{150}} - \frac{10}{150 + 50 \parallel 100} \times \frac{\frac{1}{50}}{\frac{1}{50} + \frac{1}{100}} = 0.0273 + 0.0545 - 0.0364 = 0.0455 \text{ A}$$

P2.03.

$$i = 2 \times \frac{\frac{1}{10}}{\frac{1}{10} + \frac{1}{20+40}} - 4 \times \frac{\frac{1}{10+40}}{\frac{1}{10+40} + \frac{1}{20}} + \frac{80}{20+10+40} - \frac{120}{20+10+40} = 1.71 - 1.14 - 1.14 - 1.71 = -2.29 \text{ A}$$

P2.38 using cw current

$$\begin{aligned} i_1(1+5) + 3(i_1 - i_2) &= -8 - 10 \\ i_2(4+2) + 3(i_2 - i_1) &= +6 + 10 \end{aligned} \Rightarrow \begin{aligned} i_1 &= -1.58 \text{ A} \\ i_2 &= 1.25 \text{ A} \end{aligned} \Rightarrow \begin{aligned} i_2 - i_1 &= 2.83 \\ &\Rightarrow \text{out of } + \text{ on } \\ &10 \text{ V source} \end{aligned}$$

$$P_{10} = 10 \times 2.82 = 28.3 \text{ W}$$

P2.40. $-6 + 3i + 10(i + 0.2) + 12 + 15i = 0 \Rightarrow i = -0.286 \text{ A}$

P2.47. For max power, use parallel

$$3000 = \frac{(230)^2}{R_1} + \frac{(230)^2}{R_2} = (230)^2 \left(\frac{R_1 + R_2}{R_1 R_2} \right)$$

For min power, use series

$$500 = (230)^2 / (R_1 + R_2)$$

(cont)

P2.47, cont. Simultaneous solution yields


$$R_1 = 83.4 \text{ and } 22.4$$

$$\uparrow \qquad \qquad \uparrow$$

$$R_2 = 22.4 \text{ and } 83.4$$

The four settings are
 $P_1 = 500 \text{ W}$, $P_2 = \frac{(230)^2}{83.4} = 634 \text{ W}$, $P_3 = \frac{(230)^2}{22.4} = 2366 \text{ W}$, $P_4 = 3000 \text{ W}$

4.2

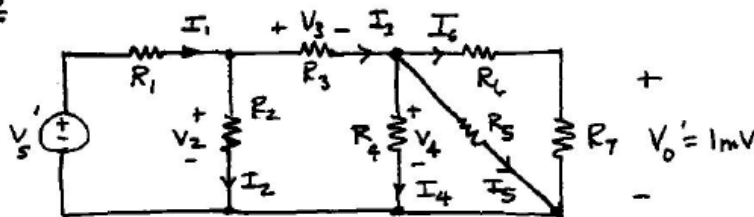

$$R_5 = 6 \text{ k}\Omega$$

All other R are $3 \text{ k}\Omega$

$$V_5 = 8 \text{ V}$$

$$I_6 = V_0' / R_7 = \frac{1}{3} \mu\text{A} \quad V_4 = I_6 (R_6 + R_7) = 2 \text{ mV} \quad I_5 = V_4 / R_5 = \frac{1}{3} \mu\text{A}$$


$$I_4 = V_4 / R_4 = \frac{2}{3} \mu\text{A} \quad I_3 = I_4 + I_5 + I_6 = \frac{4}{3} \mu\text{A} \quad V_3 = I_3 R_3 = 4 \text{ mV}$$

$$V_2 = V_3 + V_4 = 6 \text{ mV} \quad I_2 = V_2 / R_2 = 2 \mu\text{A} \quad I_1 = I_2 + I_3 = \frac{10}{3} \mu\text{A}$$

$$V_5' = I_1 R_1 + V_2 = 16 \text{ mV} \quad \frac{V_0}{V_0'} = \frac{V_5}{V_5'} \Rightarrow V_0 = \left(\frac{8}{16 \text{ mV}}\right) (1 \text{ mV}) = 0.5 \text{ V}$$

$$\boxed{V_0 = 0.5 \text{ V}}$$

4.3

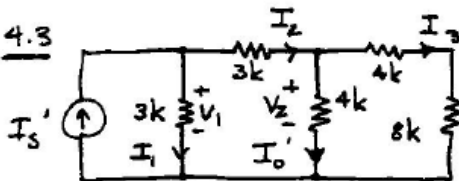

$$I_3 = 2 \text{ mA} \quad I_0' = 1 \text{ mA}$$

$$V_2 = I_0' (4 \text{ k}) = 4 \text{ V} \quad I_3 = V_2 / 12 \text{ k} = \frac{1}{3} \text{ mA}$$




$$I_2 = I_0' + I_3 = \frac{7}{3} \text{ mA}$$

$$V_1 = I_2 (3 \text{ k}) + V_2 = 8 \text{ V} \quad I_1 = V_1 / 3 \text{ k} = \frac{8}{3} \text{ mA} \quad I_s' = I_1 + I_2 = 4 \text{ mA}$$

$$\frac{I_0}{I_0'} = \frac{I_s'}{I_s'} \Rightarrow I_0 = \left(\frac{2 \text{ m}}{4 \text{ m}}\right) (1 \text{ m}) = 0.5 \text{ mA}$$

$$\boxed{I_0 = 0.5 \text{ mA}}$$



4.16

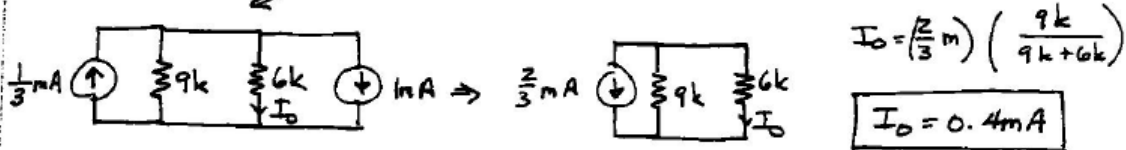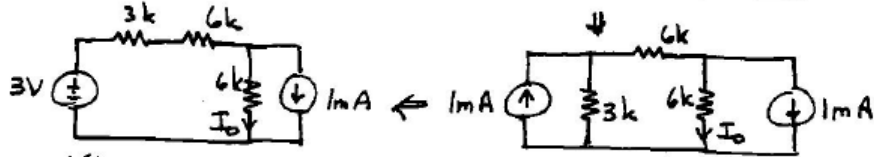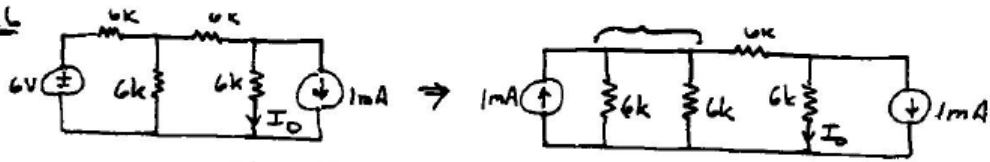

$$I_0 = \left(\frac{2}{3} \text{ m}\right) \left(\frac{9 \text{ k}}{9 \text{ k} + 6 \text{ k}}\right)$$


$$I_0 = 0.4 \text{ mA}$$

4.17

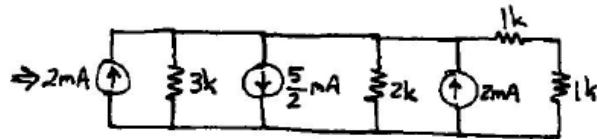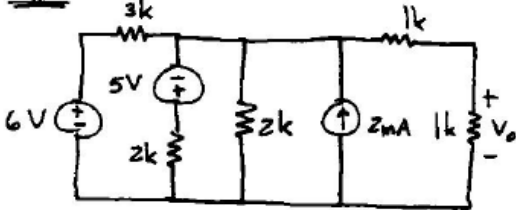

$$I_0 = 1.5 \text{ m} \left[\frac{1.2 \text{ k}}{1.2 \text{ k} + 2 \text{ k}} \right]$$
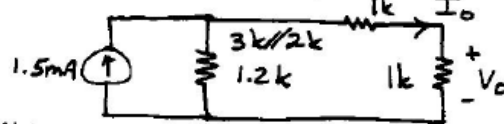
$$I_0 = 0.56 \text{ mA} \quad V_0 = I_0 (1 \text{ k}) = 0.56 \text{ V}$$



$$V_0 = 0.56 \text{ V}$$