

$$P2.08 \quad V_T = -1 \times 2 // (6+4) \times \frac{4}{4+6} = -0.667 V$$

$$R_{eq} = 4 // (6+2) = 2.67 \Omega$$

$$i = -\frac{0.667}{8+2.67} = -0.0625 A$$

$$P2.09. (a) \quad V_T = +5mA \times \left(\frac{\frac{1}{18+6}}{\frac{1}{18+6} + \frac{1}{12}} \right) \times 6k\Omega - \frac{40 \times 6}{6+18+12} \\ = 10 - 6.67 = 3.33 V$$

$$R_{eq} = 6 // (18+2) = 5 k\Omega$$

$$(b) \quad V_{ab} = 3.33 \times \frac{3}{3+5} = 1.25 V \quad (c) \quad R_L = R_{eq} = 5 k\Omega$$

$$(d) \quad V_{ab} = 0.1mA \times 6k\Omega = 0.6V = 3.33 \times \frac{R_L}{5+R_L}$$

$$\frac{5}{R_L} + 1 = \frac{3.33}{0.6} \Rightarrow R_L = 1.10 k\Omega$$

$$P2.10. \quad 10 = \frac{V_T^2}{4(20)} \Rightarrow V_T = \sqrt{800} = 28.3 V$$

$$P2.13. (a) \quad R = 6//2 = 1.50 \Omega \text{ for max power}$$

(b) Find current

$$i_{12} = \underbrace{\frac{12}{2+6//1.5}}_{\text{out of } +} - \frac{8}{6+2//1.5} \times \frac{\frac{1}{2}}{\frac{1}{2} + \frac{1}{1.5}} = 3.75 - 0.5 = 3.25 A$$

$$P_{12} = 12 \times 3.25 = 39.0 W$$

$$P2.25. \quad V : I : R_L$$

0	0.15	0
10	0.0333	300Ω
12.9	0	∞


$$\rightarrow 10 = \frac{V_T}{R_{eq} + 300} \times 300$$

but $V_T = \underbrace{0.15 R_{eq}}_{IN}$

$$\text{so } \frac{R_{eq} + 300}{0.15 R_{eq}} = \frac{300}{10} = 30 \Rightarrow R_{eq} = 85.7\Omega, V_T = 12.9 \text{ V}$$

$$I = \frac{12.9}{385.7} = 0.0333A$$

[2.34]

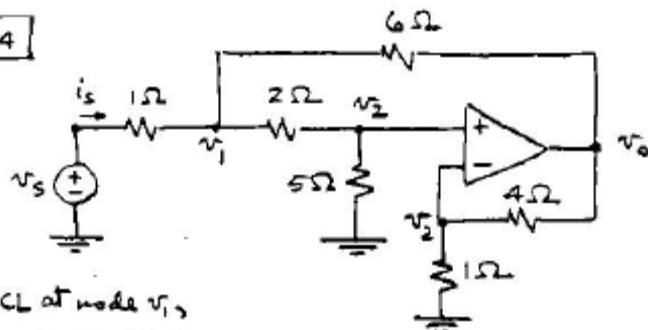

(a) By KCL at node v_1 ,

$$\frac{v_1 - v_s}{1} + \frac{v_1 - v_2}{2} + \frac{v_1 - v_o}{6} = 0$$

$$6v_1 - 6v_s + 3v_1 - 3v_2 + v_1 - v_o = 0$$

$$10v_1 - 3v_2 - v_o = 6v_s$$

$$10\left(\frac{7}{5}v_2\right) - 3v_2 - v_o = 6v_s$$

$$11v_2 - v_o = 6v_s$$

By KCL at the noninverting input of the op amp,

$$\frac{v_2 - v_1}{2} + \frac{v_2 - v_o}{5} = 0$$

$$5v_2 - 5v_1 + 2v_o = 0$$

$$7v_2 - 5v_1 = 6v_s \Rightarrow v_1 = \frac{7}{5}v_2$$

By KCL at the inverting input of the op amp,

$$\frac{v_2}{1} + \frac{v_2 - v_o}{4} = 0$$

$$4v_2 + v_2 - v_o = 0$$


$$5v_2 = v_o \Rightarrow v_2 = \frac{1}{5}v_o$$

$$11\left(\frac{1}{5}v_o\right) - v_o = 6v_s$$

$$\frac{6}{5}v_o = 6v_s$$

$$v_o = \underline{\underline{5v_s}}$$

2.36

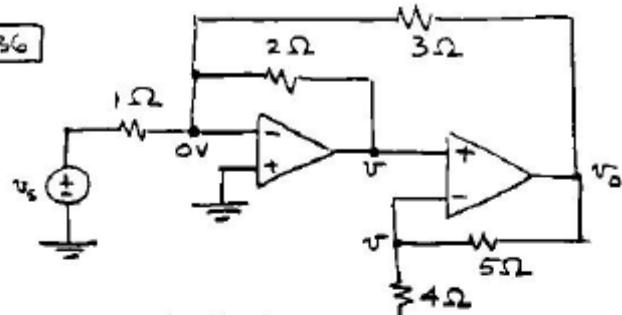

By KCL at the inverting input of the op amp on the left,

$$\frac{v_s}{1} + \frac{v}{2} + \frac{v_o}{3} = 0$$

$$6v_s + 3v + 2v_o = 0$$

By KCL at the inverting input of the op amp on the right,

$$\frac{v}{4} + \frac{v - v_o}{5} = 0$$

$$5v + 4v - 4v_o = 0$$


$$9v = 4v_o$$

$$v = \frac{4}{9}v_o$$

$$6v_s + 3\left(\frac{4}{9}v_o\right) + 2v_o = 0$$

$$6v_s = -\frac{4}{3}v_o - 2v_o = -\frac{10}{3}v_o$$
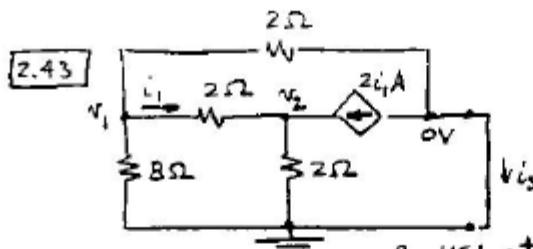
$$\therefore v_o = -\frac{3}{10}(6v_s) = -\frac{9}{5}v_s = \underline{\underline{-1.8v_s}}$$



By KCL at node v_2 ,

By KCL at node v_1 ,

$$\frac{v_1}{8} + \frac{v_1 - v_2}{2} + \frac{v_1 - v_2}{2} = 0$$

$$v_1 + 4v_1 + 4v_1 - 4v_2 = 0$$

$$9v_1 - 4v_2 = 0$$

$$3v_1 - 4v_2 = 0$$

$$6v_1 = 0$$

$$v_1 = 0V$$

$$i_1 + 2i_1 = \frac{v_2}{2}$$

$$3i_1 = \frac{v_2}{2}$$

$$3(\frac{v_1 - v_2}{2}) = \frac{v_2}{2}$$

$$3v_1 - 3v_2 = v_2$$

$$3v_1 - 4v_2 = 0$$


$$3v_1 - 4v_2 = 0$$

$$3(0) - 4v_2 = 0$$

$$-4v_2 = 0 \Rightarrow v_2 = 0V$$

By KCL,
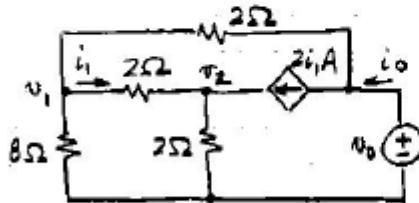
$$i_{sc} = \frac{v_1}{2} - 2i_1 = \frac{v_1}{2} - 2\left(\frac{v_1 - v_2}{2}\right) = 0A$$



By KCL at node v_{13} ,

$$\frac{v_1}{8} + \frac{v_1 - v_2}{2} + \frac{v_1 - v_0}{2} = 0$$

$$v_1 + 4v_1 - 4v_2 + 4v_1 - 4v_0 = 0$$

$$9v_1 - 4v_2 - 4v_0 = 0$$

By KCL at node v_{23} as above


$$3v_1 = 4v_2 \Rightarrow v_2 = \frac{3}{4}v_1$$


$$v_2 = \frac{1}{4}(\frac{2}{3}v_0) = \frac{1}{6}v_0$$

$$\text{By KCL, } i_0 = 2i_1 + \frac{v_0 - v_1}{2} = 2\left(\frac{v_1 - v_2}{2}\right) + \frac{v_0 - v_1}{2} = \frac{2}{3}v_0 - \frac{1}{2}v_1 + \frac{v_0 - \frac{2}{3}v_0}{2}$$

$$i_0 = \frac{2}{3}v_0 - \frac{1}{2}v_1 \approx \frac{1}{3}v_0$$
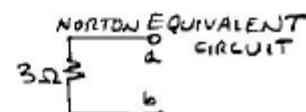
$$\therefore R_o = \frac{v_0}{i_0} = \frac{3}{1} \Omega$$



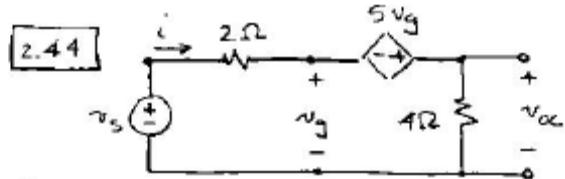


$$\text{By KVL, } v_s = 2i - 5v_g + 4i \quad \text{Also, } -v_g - 5v_g + 4i = 0$$

$$v_s = 6i - 5v_g \quad 4i = 6v_g \Rightarrow v_g = \frac{2}{3}i$$

$$v_s = 6i - 5\left(\frac{2}{3}i\right) = 6i - \frac{10}{3}i = \frac{8}{3}i \Rightarrow i = \frac{3}{8}v_s$$

By Ohm's law,
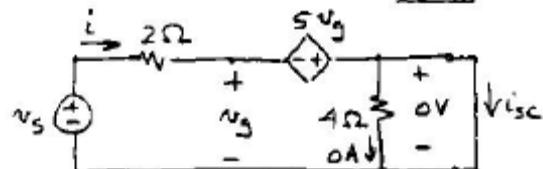
$$v_{oc} = 4i = 4\left(\frac{3}{8}v_s\right) = \underline{\underline{\frac{3}{2}v_s}}$$



$$\text{By KVL, } v_s = 2i - 5v_g \quad \text{Also, } -v_g - 5v_g = 0$$

$$-6v_g = 0 \Rightarrow v_g = 0V$$

$$\therefore v_s = 2i \Rightarrow i = \frac{1}{2}v_s$$

By KCL,

$$i_{sc} = i = \frac{1}{2}v_s$$

$$\therefore R_0 = \frac{v_{oc}}{i_{sc}} = \frac{\frac{3}{2}v_s}{\frac{1}{2}v_s} = \underline{\underline{3\Omega}}$$

Thus, the Thévenin-equivalent circuit is

