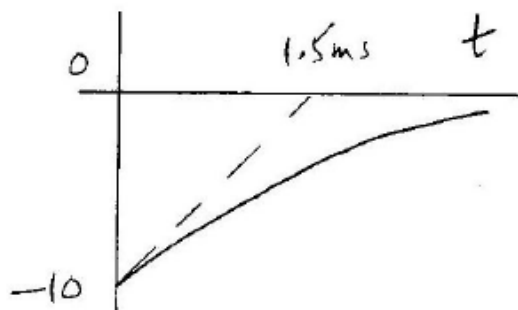


P3.17 $\tau = \frac{L}{R} = \frac{1.5}{1000} = 1.5 \text{ms}$ $v_L(\infty) = 0$, $v_L(0) = -10 \text{mA} \times 1000 \Omega = -10 \text{V}$


$$v_L(t) = 0 + (-10 - 0)e^{-t/1.5 \text{ms}} \text{ V}$$



P3.18(a) $\tau = \frac{L}{R} = \frac{0.2 \text{mH}}{10^4} = 2 \times 10^{-8} = 20 \text{ns}$

$i(0) = 10 \text{mA}$, $i(\infty) = 0$ so (b) $i_{sw} = 10(1 - e^{-t/20 \text{ns}}) \text{ mA}$
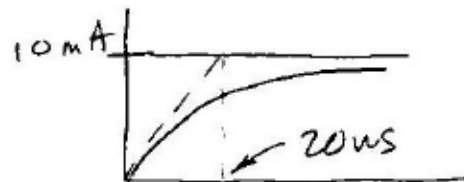
$$i = 0 + (10 - 0)e^{-t/20 \text{ns}} \text{ mA}$$



$$P3.19 \text{ (a)} \quad \tau = 1\mu\text{F} \times 100\Omega = 100\mu\text{s}$$

$$i(0) = \frac{100\text{V}}{100\Omega} = 1\text{A}, \quad i(\infty) = 0$$

$$i(t) = 1 e^{-t/100\mu\text{s}} \text{ A}$$

$$(b) \quad p_R = i^2 R = 100 e^{-2t/100\mu\text{s}} \Rightarrow W_R = \int_0^{\infty} 100 e^{-2t/100\mu\text{s}} dt$$

$$W_e = \frac{1}{2} C v_c^2(0) = \frac{1}{2} \times 10^{-6} (100)^2 = + \frac{1}{200} \text{ J}$$

$$= \frac{1}{2} \times 10^{-2} \text{ J} \quad \leftarrow \text{SAME}$$

$$P3.21. \text{ (a)} \quad \tau = 1200 \times 5\mu\text{F} = 6000\mu\text{s} = 6\text{ms}$$

$$v_{sw}(0) = 0 \text{ since capacitor is charged to } +10\text{V.}$$

$$v_{sw}(\infty) = +10\text{V since } v_c \rightarrow 0$$

$$v_{sw} = 10 + (0 - 10) e^{-t/6\text{ms}}$$

P3.35.

$$\tau = 100\mu\text{F} \times (10 \parallel 30) = 0.75 \text{ ms}$$

$$v(0) = +50\text{V}$$

$$v(\infty) = 50 \times \frac{10}{10+30} = +12.5\text{V}$$

$$\Rightarrow v(t) = 12.5 + (50 - 12.5) e^{-t/0.75}$$

$$W_e = \frac{1}{2} \times 100\mu\text{F} \times (37.5)^2 = 70.3 \text{ mJ}$$

P3.38. Switch closed; $\tau = 10\mu\text{F} \times (2\text{k}\Omega \parallel 2\text{k}\Omega) = 10\text{ms}$

$$i(0) = 0$$

$$i(\infty) = \frac{10\text{V}}{2+2\text{k}\Omega} = 2.5\text{mA} \Rightarrow i(t) = 2.5(1 - e^{-t/10\text{ms}}) \text{ mA}$$


Switch open: $\tau = 10\mu\text{F} \times 2\text{k}\Omega = 20\text{ms}$

$$i("0") = 2.5(1 - e^{-5/10}) = 0.984\text{mA}$$

$$i(\infty) = 0$$

so
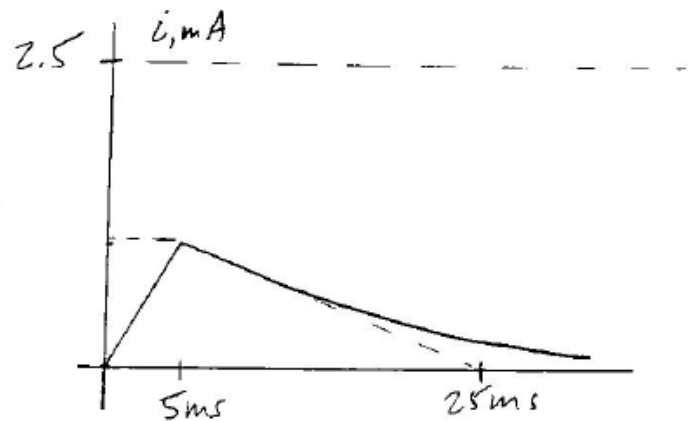
$$i(t) = 0.984 e^{-t'/20\text{ms}} \text{ mA}$$
$$= 0.984 e^{-(t-5\text{ms})/20\text{ms}}$$



P3.39. switch closed $\tau = \frac{0.2}{125 \parallel 500} = 2 \text{ ms}$

$$v(0) = 120 \times \frac{125}{125+500} = 24 \text{ V}$$

$$v(\infty) = 0 \text{ V} \Rightarrow v(t) = 24 e^{-t/2 \text{ ms}} \text{ V}$$

We also need $i_L = \frac{120}{500} (1 - e^{-t/2 \text{ ms}}) = 0.0944 \text{ A}$ at $t = 1 \text{ ms}$

Switch open: $\tau = \frac{0.2}{125} = 1.6 \text{ ms}$

$$v(0) = -0.944 \times 125 = -11.8 \text{ V}$$

$$v(\infty) = 0 \Rightarrow v(t) = -11.8 e^{-t'/1.6 \text{ ms}}$$

