
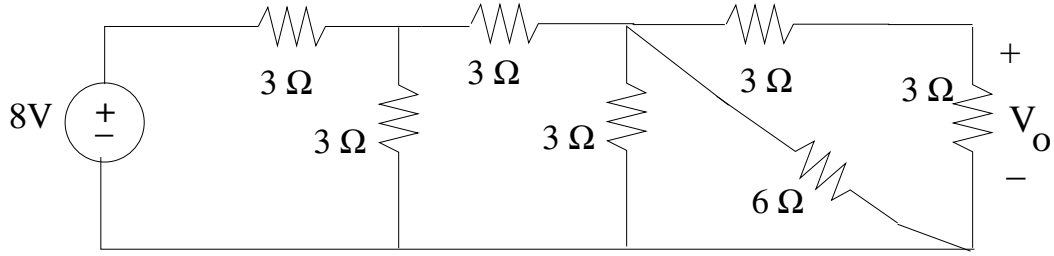



Problem 1: Find V_o in the following circuit using linearity and the assumption that $V_o = 1V$.

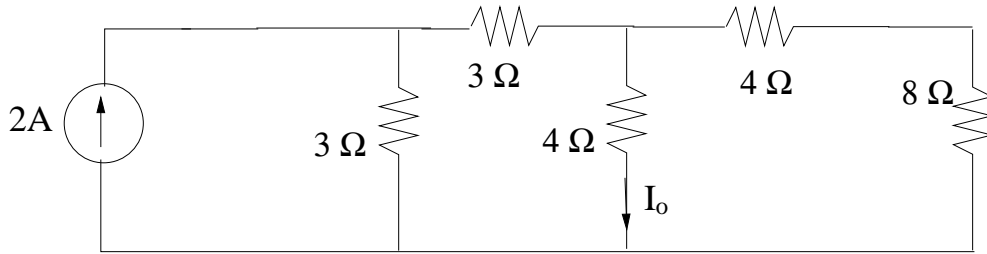

Problem 2: Find I_o in the following circuit using linearity and the assumption that $I_o = 1A$.



Problem 3: Find I_o in the following circuit using source transformation.

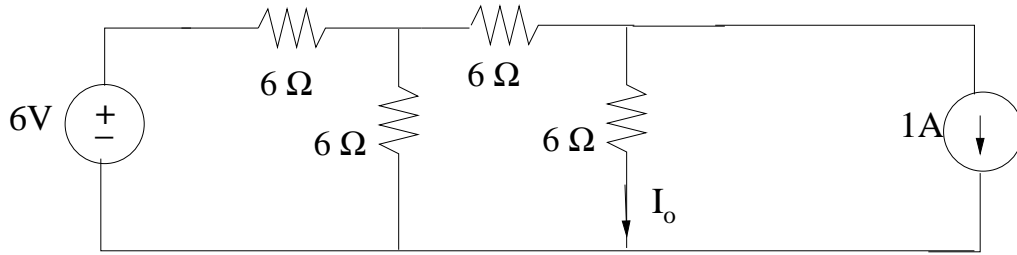

Problem 4: Find V_o in the following circuit using source transformation.

