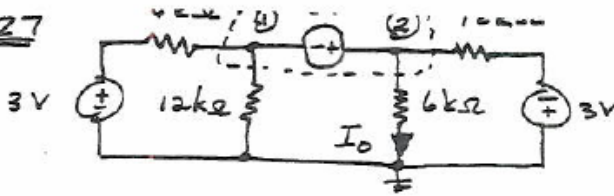


3.27



Use the supernode encircled by the dotted line!

At supernode: 
$$\frac{V_1 - 3}{6000} + \frac{V_1}{12,000} + \frac{V_2}{6,000} + \frac{V_2 + 3}{12,000} = 0$$

$$2V_1 - 6 + V_1 + 2V_2 + V_2 + 3 = 0$$

$$3V_1 + 3V_2 = 3 \Rightarrow V_1 + V_2 = 1 \quad (1)$$


Constraint:  $V_2 - V_1 = 6 \Rightarrow V_1 = V_2 - 6 \quad (2)$

Substitute (2) into (1) & find  $V_2$ ,

$$V_2 - 6 + V_2 = 1 \Rightarrow 2V_2 = 7 \Rightarrow V_2 = 3.5V$$

$$I_0 = V_2 / 6,000 \Rightarrow \boxed{I_0 = 0.58 \text{ mA}}$$

3.45

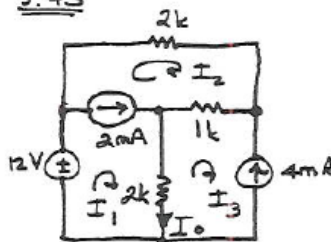

$$12 = (2k)I_2 + 1k(I_2 - I_3) + 2k(I_1 - I_3)$$


$$12 = (3k)I_2 + 2kI_1 - 3kI_3 \quad (1)$$

$$I_2 = I_1 - \frac{2}{1000} ; I_3 = -\frac{4}{1000} \quad (2) \text{ \& } (3)$$



Substitute (2) & (3) into (1):  $12 = (5k)I_1 + 6$

$$I_1 = \frac{6}{5} \text{ mA} \Rightarrow I_0 = I_1 - I_3 = \frac{6}{5} + 4 \text{ mA} \quad \boxed{I_0 = 5.2 \text{ mA}}$$


4.21

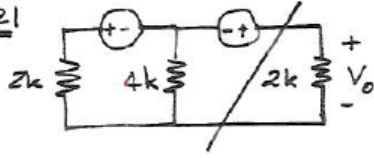

Find  $R_{TH}$

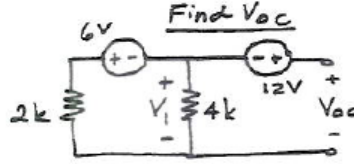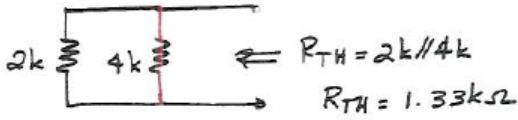

$$V_{OC} = 12 + V_1 = 8V$$

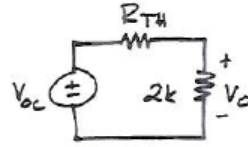

$$V_1 = -6 \left[ \frac{4k}{4k+2k} \right]$$

$$V_1 = -4V$$

$$V_o = V_{OC} \left( \frac{2k}{2k+R_{TH}} \right)$$

$$V_o = 4.8V$$