

Course: ECE 53a  
Quiz #2  
Instructor: Pamela Cosman  
Date: 2/21/07

Name: \_\_\_\_\_

There are 3 problems.

The first two problems are worth 12 points each. The last problem is worth 16 points.


Problem	Possible	Score
1	12	
2	12	
3	16	
Total	40	

This quiz is **CLOSED BOOK, NO CALCULATORS ALLOWED.**


You may use one page of notes, 8.5 by 11, both sides, written by you.

You need to show your work for all problems.

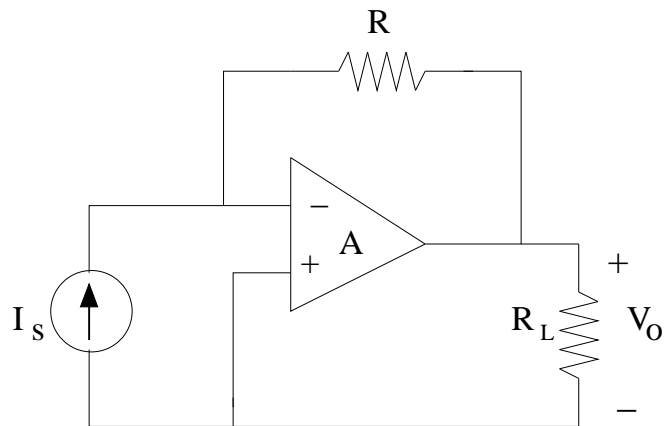Problem 1: The following circuit is a current-to-voltage converter. The amplifier has a finite gain  $A = 100$ . Select the resistance  $R$  so that the output voltage  $V_o$  has a magnitude of  $0.1 \text{ V}$  per  $\mu\text{A}$  of input current  $I_s$ .




**Problem 2:** Determine the output voltage  $V_o$  for the following circuit, in terms of the input voltages  $V_a$  and  $V_b$  and the resistor values  $R$  and  $R_1$ . Assume the amplifier is an ideal op amp.

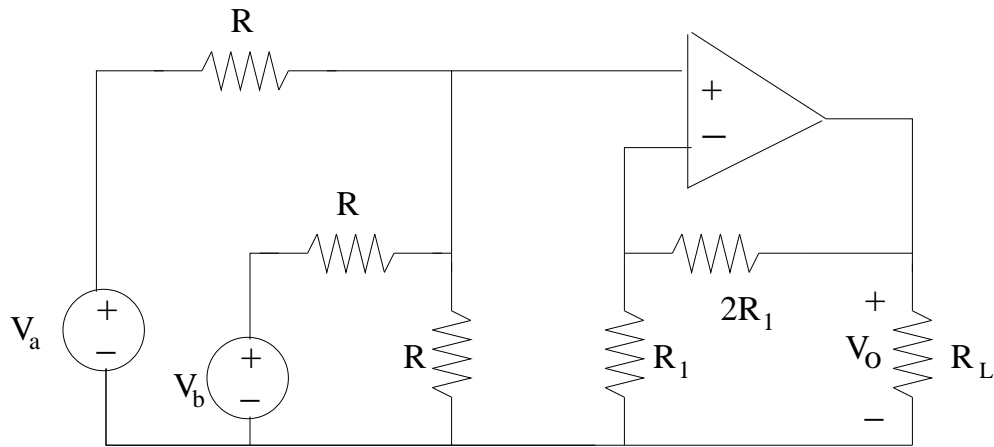

**Problem 3:**

For the following circuit, assume that the switch is to the left since  $t = -\infty$ .

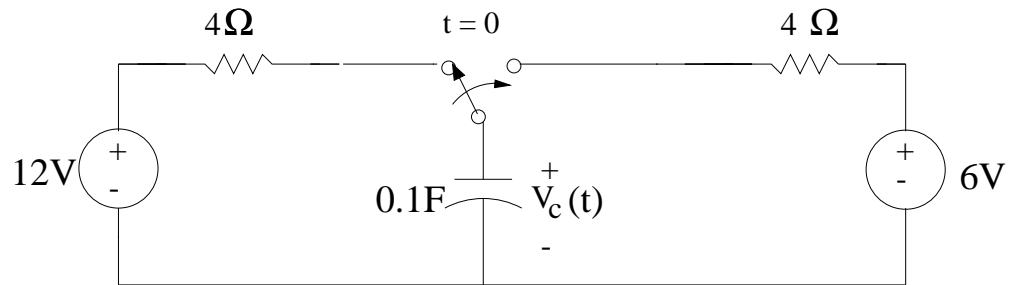(a) Suppose the switch switches over to the right at  $t = 0$ . Find the voltage across the capacitor,  $V_C(t)$ , for all  $t$ .



(b) Suppose the switch, after having moved over to the right at  $t = 0$ , were to go back to the left at  $t = 0.2s$ . Find an expression for the voltage across the capacitor,  $V_C(t)$ , for  $t > 0.2s$ .

