
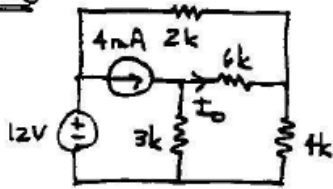


4.26

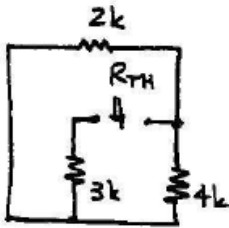


Find R_{TH}



$$R_{TH} = 3k + (2k // 4k)$$

$$R_{TH} = 4.33k\Omega$$

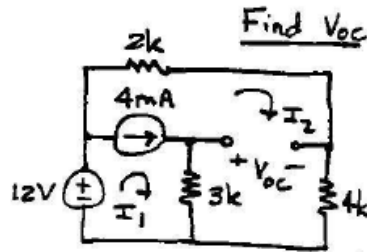

Find V_{OC}

$$I_1 - I_2 = 4mA$$

$$12 = (2k)I_2 + 4k(I_2)$$

$$\text{So, } I_2 = 2mA \text{ \& } I_1 = 6mA$$

$$V_{OC} = 3k(I_1 - I_2) - 4k(I_2)$$

$$V_{OC} = 4V$$


$$I_0 = \frac{V_{OC}}{R_{TH} + 4k}$$

$$I_0 = 0.39mA$$

P2.17. $R_{eq} = 6\Omega$ and $100 = \frac{V_T^2}{4 \times 6} \Rightarrow V_T = 49.0V$

$$i = \frac{49.0}{6+3} = 5.44A$$

2.33

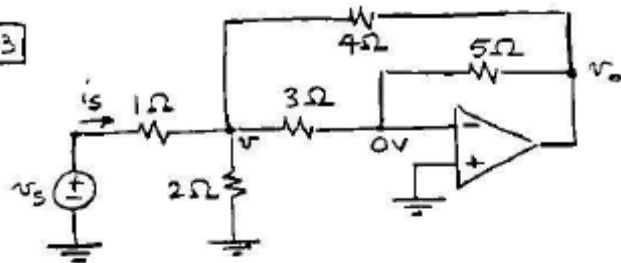

(a)

By KCL at node v ,

$$\frac{v - v_s}{1} + \frac{v}{2} + \frac{v}{3} + \frac{v - v_o}{4} = 0$$

$$12v - 12v_s + 6v + 4v + 3v - 3v_o = 0$$

$$25v - 3v_o = 12v_s$$

$$25\left(-\frac{3}{5}v_o\right) - 3v_o = 12v_s$$

$$-15v_o - 3v_o = 12v_s$$

$$-18v_o = 12v_s$$

$$v_o = -\frac{12}{18}v_s = -\frac{2}{3}v_s$$

By KCL at the inverting input of the op-amp,

$$\frac{v}{3} + \frac{v_o}{5} = 0$$

$$5v + 3v_o = 0$$

$$5v = -3v_o$$


$$v = -\frac{3}{5}v_o$$

(b) $v = -\frac{3}{5}v_o = -\frac{3}{5}\left(-\frac{2}{3}v_s\right) = \frac{2}{5}v_s$

$$i_s = \frac{v_s - v}{1} = \frac{v_s - \frac{2}{5}v_s}{1} = \frac{3}{5}v_s$$

$$\therefore R_{in} = \frac{v_s}{i_s} = \frac{5}{3} \Omega$$

2.33

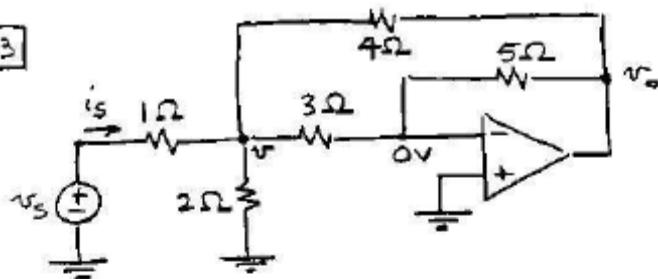

(a)

By KCL at node v ,

$$\frac{v - v_s}{1} + \frac{v}{2} + \frac{v}{3} + \frac{v - v_o}{4} = 0$$

$$12v - 12v_s + 6v + 4v + 3v - 3v_o = 0$$

$$25v - 3v_o = 12v_s$$

By KCL at the inverting input of the op-amp,

$$\frac{v}{3} + \frac{v_o}{5} = 0$$

$$5v + 3v_o = 0$$

$$5v = -3v_o$$

$$v = -\frac{3}{5}v_o$$

$$25\left(-\frac{3}{5}v_o\right) - 3v_o = 12v_s$$

$$-15v_o - 3v_o = 12v_s$$

$$-18v_o = 12v_s$$

$$v_o = -\frac{12}{18}v_s = -\frac{2}{3}v_s$$

$$(b) v = -\frac{3}{5}v_o = -\frac{3}{5}\left(-\frac{2}{3}v_s\right) = \frac{2}{5}v_s$$

$$i_s = \frac{v_s - v}{1} = \frac{v_s - \frac{2}{5}v_s}{1} = \frac{3}{5}v_s$$

$$\therefore R_{in} = \frac{v_s}{i_s} = \frac{5}{3} \Omega$$