


(a) $v_R(t) = L \frac{di(t)}{dt} = 2 \frac{di(t)}{dt} = \begin{cases} 0 & \text{for } t \leq 0 \\ -2 & \text{for } 0 < t \leq 1 \\ 2 & \text{for } 1 < t \leq 2 \\ 0 & \text{for } t > 2 \end{cases}$

(b) $v_L(t) = \frac{1}{2} L i^2(t) = i^2(t) = \begin{cases} 0 & \text{for } t \leq 0 \\ t^2 & \text{for } 0 < t \leq 1 \\ (t-2)^2 & \text{for } 1 < t \leq 2 \\ 0 & \text{for } t > 2 \end{cases}$

(c) $\rho_R(t) = R i^2(t) = 2 i^2(t) = \begin{cases} 0 & \text{for } t \leq 0 \\ 2t^2 & \text{for } 0 < t \leq 1 \\ 2(t-2)^2 & \text{for } 1 < t \leq 2 \\ 0 & \text{for } t > 2 \end{cases}$

(d) $v_R(t) = R i(t) = 2i(t) = \begin{cases} 0 & \text{for } t \leq 0 \\ -2t & \text{for } 0 < t \leq 1 \\ 2(t-2) & \text{for } 1 < t \leq 2 \\ 0 & \text{for } t > 2 \end{cases}$

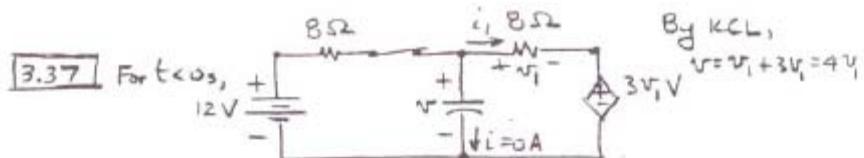(e) $v_s(t) = v_R(t) + v_L(t) = \begin{cases} 0 & \text{for } t \leq 0 \\ -2t-2 & \text{for } 0 < t \leq 1 \\ 2t-2 & \text{for } 1 < t \leq 2 \\ 0 & \text{for } t > 2 \end{cases}$




For dc, the capacitor is an open circuit. Thus, $i(t) = 0A$.

$$\text{By KVL, } 12 = 8i_1 + v_1 + 3v_1 = 8i_1 + 4v_1 = 8i_1 + 4(3i_1) = 40i_1$$

$$\therefore i_1 = \frac{12}{40} = 0.3A \Rightarrow v_1 = 8i_1 = 8(0.3) = 2.4V$$

$$\therefore v(t) = 4v_1(t) = 4(2.4) = 9.6V$$

Thus, $v(0) = 9.6V$

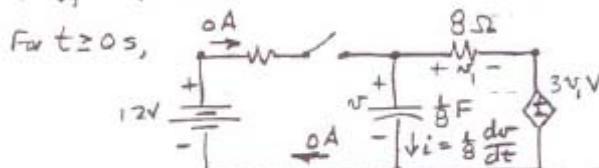

$$\text{By KVL, } v - 3v_1 - v_1 = 0 \quad \text{By Ohm's law, } v_1 = -8i$$

$$v - 4v_1 = 0$$

$$v - 4(-8i) = 0$$



$$v + 32\left(\frac{1}{8}\frac{dv}{dt}\right) = 0$$

$$\frac{dv}{dt} + \frac{1}{4}v = 0 \Rightarrow v(t) = v(0)e^{-t/4} = 9.6e^{-t/4} V$$


$$\text{Thus, } i(t) = \frac{1}{8} \frac{dv(t)}{dt} = \frac{1}{8} \frac{d}{dt}(9.6e^{-t/4}) = -0.3e^{-t/4} A$$

Hence,
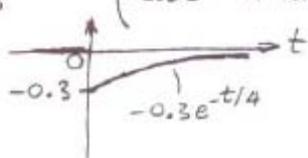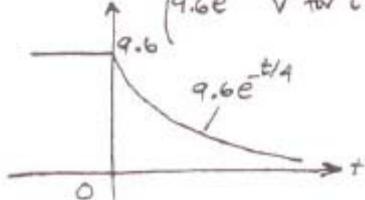
$$v(t) = \begin{cases} 9.6V & \text{for } t < 0s \\ 9.6e^{-t/4}V & \text{for } t \geq 0s \end{cases} \quad i(t) = \begin{cases} 0A & \text{for } t < 0s \\ -0.3e^{-t/4}A & \text{for } t \geq 0s \end{cases}$$



6.8

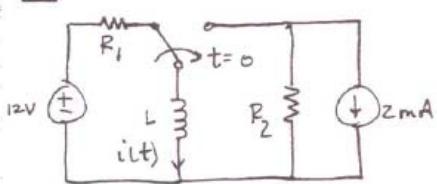

$$R_1 = 6\text{k}\Omega$$

when $t < 0$,


$$R_2 = 4\text{k}\Omega$$

$$L = 0.2\text{mH}$$

$$i(0^-) = i(0^+) = \frac{12}{R_1} = 2\text{mA}$$

For $t > 0$
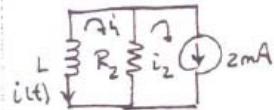
$$\text{KVL: } L \frac{di_1(t)}{dt} + R_2(i_1 - i_2) = 0 \quad \text{if } i_2 = 2\text{mA}$$



$$\frac{di_1(t)}{dt} + \frac{R_2}{L} i_1 = \frac{R_2}{L} i_2$$

$$\text{Assume } i_1(t) = K_1 + K_2 e^{-t/\tau}, \text{ now, } -\frac{K_2}{\tau} e^{-t/\tau} + \frac{R_2}{L} K_1 + \frac{R_2}{L} K_2 e^{-t/\tau} = \frac{R_2}{L} i_2$$

$$\text{Yields } \tau = L/R_2 = 50\text{ns} \text{ and } K_1 = 2\text{mA}.$$

$$i_1(0) = -i_2(0) = -2\text{mA} = K_1 + K_2 \Rightarrow K_2 = -4\text{mA}. \text{ Also, } i_1(t) = -i_2(t)$$

$$i_1(t) = (4e^{-2 \times 10^8 t} - 2)\text{mA} \text{ for } t \geq 0 \text{ and } i_1(t) = 2\text{mA} \quad t < 0$$